



UNITED INTERNATIONAL UNIVERSITY (UIU)

Dept. of Computer Science & Engineering

Trimester: Summer 2021

Course No: EEE 2123

Title: Electronics

Section E

Class Test-04

Total marks = 30

Duration : 35+10= 45 minutes total


1) Consider the following circuit:

3*6=18

X= last Digit of your ID

Y= 2nd last digit of your ID

Z= 3rd last digit of your ID

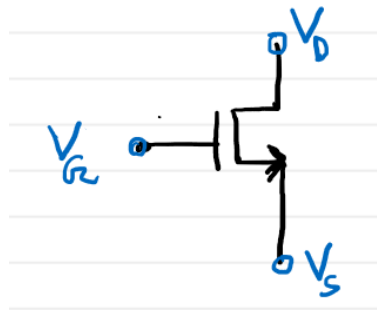

Case 1)

$V_G = X$ Volt,

$V_D = Y$ Volt,

$V_t = 2$ V

Determine Maximum Source Voltage so that, MOSFET remain in cut off mode

Case 2)

$V_D = Z$ Volt,

$V_t = 0.5$ V

$V_S = -1$ Volt,

Determine the Gate voltage so that circuit operates at the edge of saturation

Case 3)

$V_G = X$ Volt,

$V_t = 3$ Volt


$V_S = (X - V_t - 1)$ Volt,

Determine the maximum Drain voltage so that circuit operates in triode region

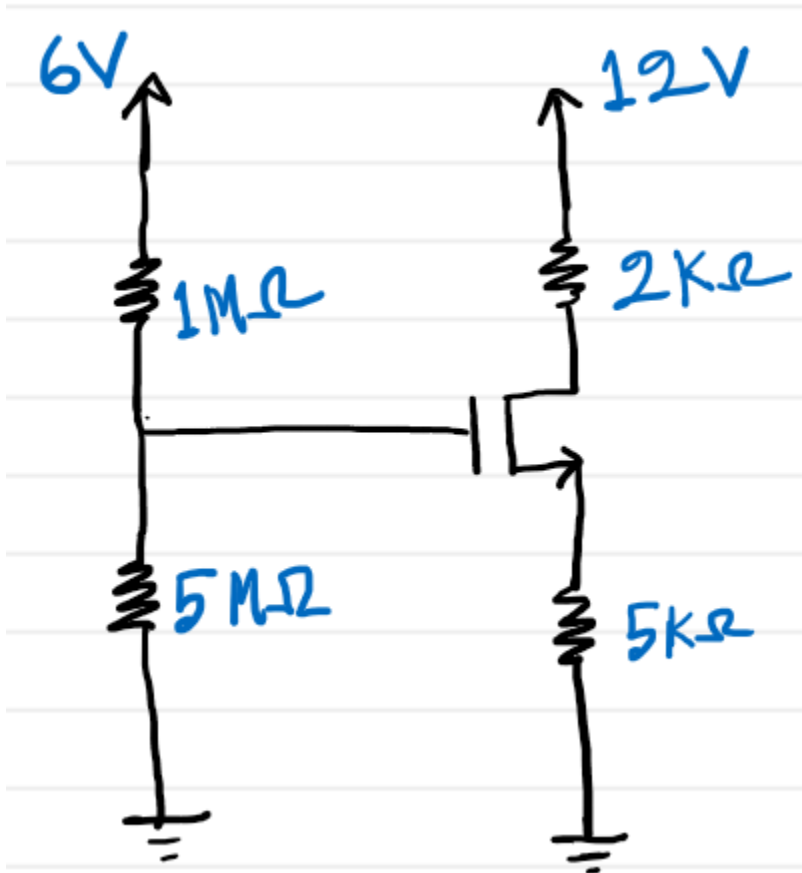2) Consider the following circuit:

12

$$V_t = \log_{10} (\text{last digit of your ID}/2 + 2)$$



The MOSFET is operating with $K_n' = 1 \text{ mA/V}^2$, $W/L = 2 \mu\text{m} / 1 \mu\text{m}$;

Find the mode of operation and values of and voltage at drain, source and gate